

**NANYANG TECHNOLOGICAL UNIVERSITY****SEMESTER 1 EXAMINATION 2022-2023****EE2101 – CIRCUIT ANALYSIS**


November / December 2022

Time Allowed: 2 hours

**INSTRUCTIONS**

1. This paper contains 4 questions and comprises 7 pages.
  2. Answer all 4 questions.
  3. All questions carry equal marks.
  4. This is a closed book examination.
  5. Unless specifically stated, all symbols have their usual meanings.
  6. The Laplace Transform Table is provided in Appendix A on pages 6 and 7.
- 


1. (a) Using Mesh analysis, determine the currents  $i_1$  and  $i_2$  of the circuit in Figure 1.1. Hence, determine the power supplied by the current source.

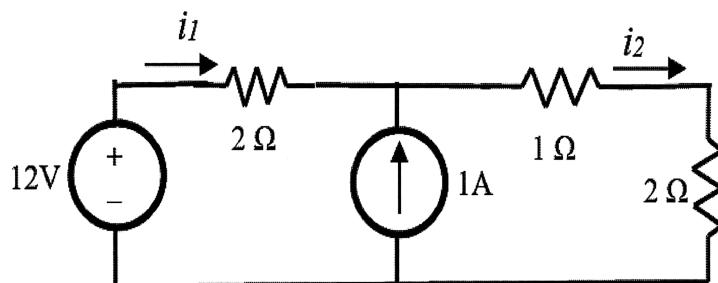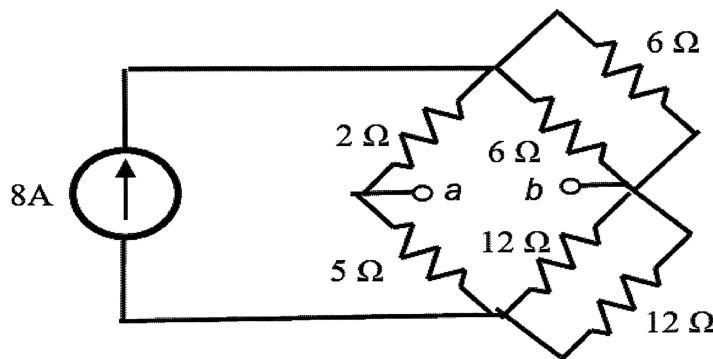**Figure 1.1**

(11 Marks)


Note: Question No. 1 continues on page 2.

- (b) Find the Thevenin equivalent of the terminal  $a, b$  of the circuit in Figure 1.2. If a resistor is connected to the terminals  $a, b$ , determine the maximum power that can be delivered to the resistor.

**Figure 1.2**

(14 Marks)


2. (a) Consider the circuit in Figure 2.1 where the switch  $S$  has been at position  $a$  for a very long time. The switch is moved to position  $b$  at  $t = 0$ . Using time domain analysis, determine the voltage  $v(t)$  for  $t > 0$ .

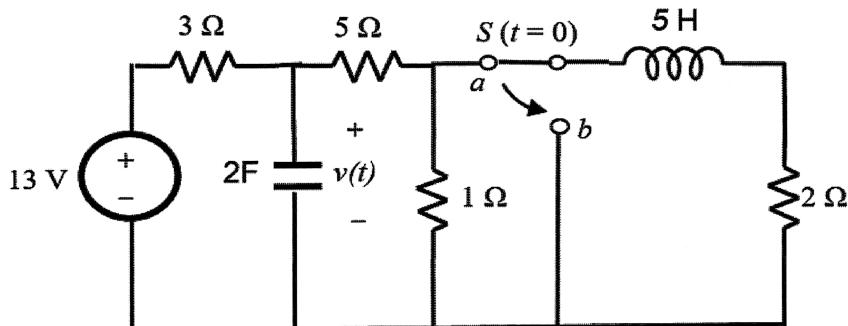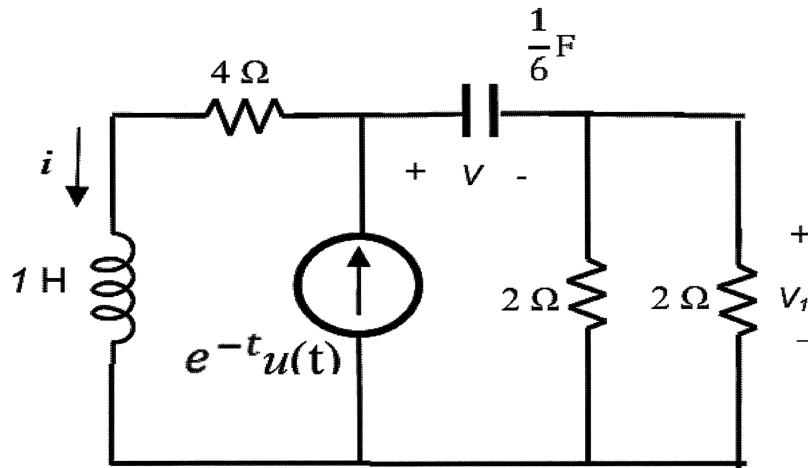**Figure 2.1**

(12 Marks)


Note: Question No. 2 continues on page 3.

- (b) Given  $v(0) = 0 \text{ V}$ ,  $i(0) = 0 \text{ A}$  and  $u(t)$  is a unit step function, determine  $i(t)$  of the circuit in Figure 2.2 by using s-domain analysis. Hence, determine  $v_1(t)$ .

**Figure 2.2**

(13 Marks)

3. (a) The circuit in Figure 3.1 is designed such that the 50 Hz voltage source delivers maximum power to the load modeled by the resistor  $R$ . Find the values of resistor  $R$  and capacitor  $C$  for maximum power to be delivered to the load. Hence, find the maximum power absorbed by the load.

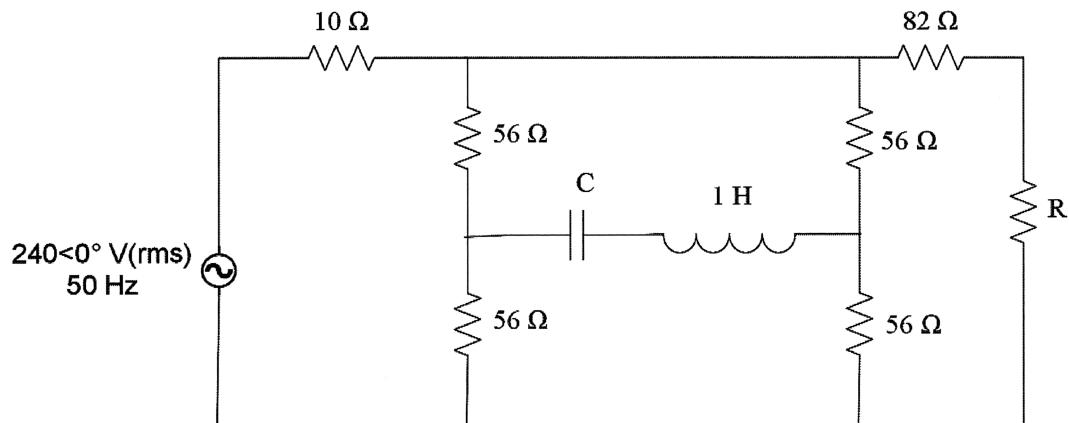
**Figure 3.1**

(12 Marks)


Note: Question No. 3 continues on page 4.

- (b) Electrical power is delivered to a Gunmetal Manufacturing Facility as shown in Figure 3.2. The frequency of voltage source is 50 Hz. The Gunmetal Manufacturing Facility has the following loads:

- Inductive loads absorbing 13700 kVAR at a power factor of 0.65 lagging.
- Highly resistive loads absorbing 9900 kW at a power factor of 0.95 lagging.
- Capacitive loads absorbing 770 kVA at a power factor of 0.55 leading.

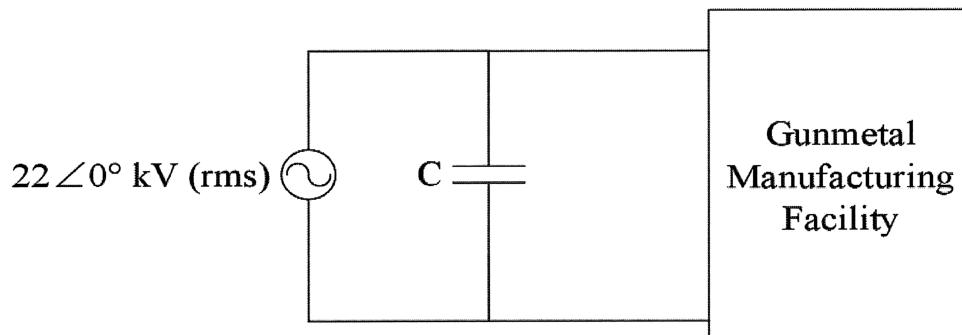**Figure 3.2**


- (i) Find the total complex power of the Gunmetal Manufacturing Facility.  
(ii) Find the reactive power supplied by the capacitor C in Figure 3.2 that will correct the power factor to 0.97 lagging as seen by the 22 kV voltage source.
- (13 Marks)
4. (a) Find the ABCD parameters of the network shown in Figure 4.1. Using the ABCD parameters show that the network is reciprocal.

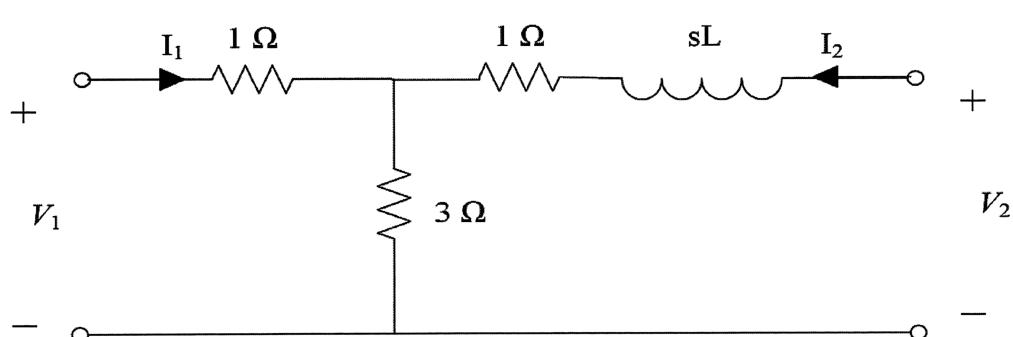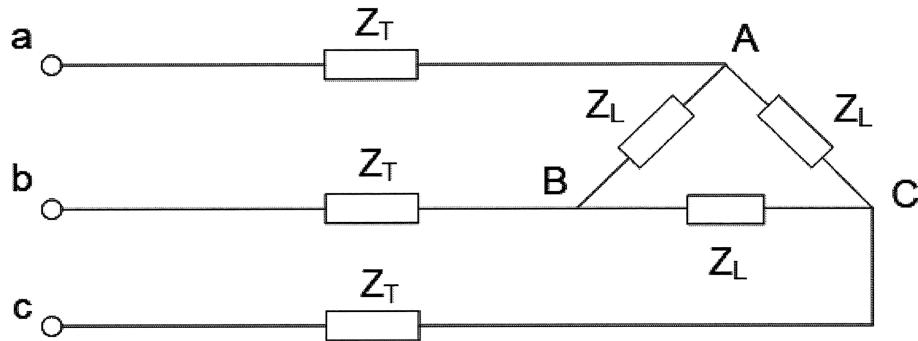**Figure 4.1**

(12 Marks)

Note: Question No. 4 continues on page 5.

- (b) Figure 4.2 shows a balanced 50 Hz delta-connected source with rms voltages ( $V_{ab} = 415 \angle 25^\circ$  V,  $V_{bc} = 415 \angle -95^\circ$  V,  $V_{ca} = 415 \angle -215^\circ$  V) supplying power to a balanced delta-connected load. The phase load is  $Z_L = (843 + j489)$  Ω and the transmission line impedance is  $Z_T = (2 + j5)$  Ω. Find the line currents and the total reactive power absorbed by the delta-connected load.

**Figure 4.2**

(13 Marks)

**Appendix A**  
**Laplace Transform Table**

	$f(t)$	$F(s)$
1. Unit impulse	$\delta(t)$	1
2. Unit step	$u(t)$	$\frac{1}{s}$
3. Unit ramp	$r(t) = tu(t)$	$\frac{1}{s^2}$
4. Unit parabola	$p(t) = \frac{1}{2}t^2u(t)$	$\frac{1}{s^3}$
5. Exponential	$e^{-at}$	$\frac{1}{s+a}$
6. t-Multiplication exponential	$te^{-at}$	$\frac{1}{(s+a)^2}$
7. Sine	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
8. Cosine	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
9. Damped Sine	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
10. Damped Cosine	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
11. Linearity	$c_1f_1(t) + c_2f_2(t)$	$c_1F_1(s) + c_2F_2(s)$
12. Differentiation	$\frac{d}{dt}f(t)$	$sF(s) - f(0)$
13. n-Fold differentiation	$\frac{d^n}{dt^n}f(t)$	$s^n F(s) - s^{n-1}f(0) - s^{n-2}f'(0) - \dots - sf^{(n-2)}(0) - f^{(n-1)}(0)$
14. Integration	$\int_{0-}^t f(\tau)d\tau$	$\frac{F(s)}{s}$
15. t-Multiplication	$tf(t)$	$\frac{-d}{ds}F(s)$

Note: Laplace Transform Table continues on page 7.

**Appendix A (continued)**  
**Laplace Transform Table (continued)**

	$f(t)$	$F(s)$
16. n-Fold t-Multiplication	$t^n f(t)$	$(-1)^n \frac{d^n}{ds^n} F(s)$
17. Time shift	$f(t - t_0)u(t - t_0);$ $t_0 > 0$	$e^{-st_0} F(s)$
18. Frequency shift	$e^{-s_0 t} f(t)$	$F(s + s_0)$
19. Time-frequency scaling	$f(ct) ; c > 0$	$\frac{1}{c} F\left(\frac{s}{c}\right)$
20. Periodic Function	$f(t) = f_1(t)u(t)$ $+ f_1(t-T)u(t-T)$ $+ f_1(t-2T)u(t-2T) + \dots$	$\frac{1}{1 - e^{-sT}} F_1(s)$

END OF PAPER

# **EE2101 CIRCUIT ANALYSIS**

Please read the following instructions carefully:

- 1. Please do not turn over the question paper until you are told to do so. Disciplinary action may be taken against you if you do so.**
2. You are not allowed to leave the examination hall unless accompanied by an invigilator. You may raise your hand if you need to communicate with the invigilator.
3. Please write your Matriculation Number on the front of the answer book.
4. Please indicate clearly in the answer book (at the appropriate place) if you are continuing the answer to a question elsewhere in the book.