

NANYANG TECHNOLOGICAL UNIVERSITY**SEMESTER 2 EXAMINATION 2023-2024****EE2101 – CIRCUIT ANALYSIS**


April / May 2024

Time Allowed: 2 hours

INSTRUCTIONS

1. This paper contains 4 questions and comprises 7 pages.
 2. Answer all 4 questions.
 3. All questions carry equal marks.
 4. This is a closed book examination.
 5. Unless specifically stated, all symbols have their usual meanings.
 6. The Laplace Transform Table is provided in Appendix A on pages 6 and 7.
-


1. (a) Using Nodal analysis, determine the voltages v_1 and v_2 of the circuit in Figure 1.1. Hence, determine the power of the independent current source.

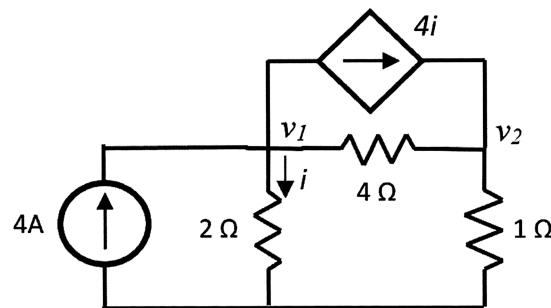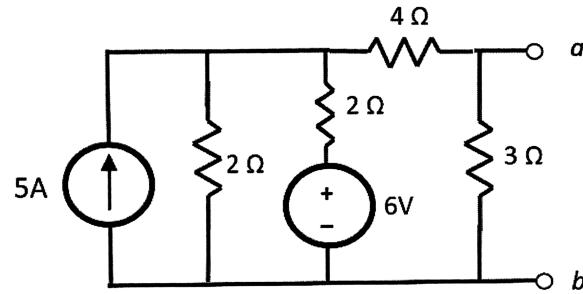**Figure 1.1**

(12 Marks)


Note: Question No. 1 continues on page 2.

- (b) Find the Thevenin equivalent of the terminal a , b of the circuit in Figure 1.2.

**Figure 1.2**

(13 Marks)


2. (a) Consider the circuit in Figure 2.1 where the switch S has been at position a for a very long time. The switch is moved to position b at $t = 0$. Using time domain analysis, determine the current $i(t)$ for $t > 0$.

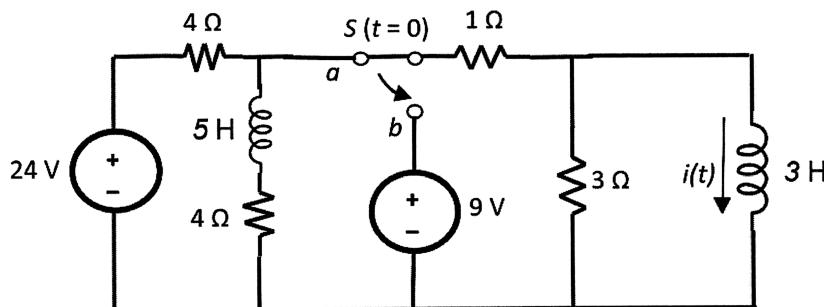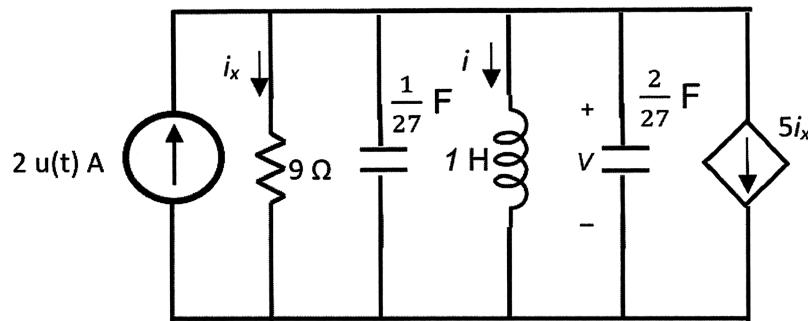**Figure 2.1**

(13 Marks)


Note: Question No. 2 continues on page 3.

- (b) Given $v(0) = 0$ V, $i(0) = 0$ A and $u(t)$ is a unit step function, determine $v(t)$ of the circuit in Figure 2.2 by using s-domain analysis.

**Figure 2.2**

(12 Marks)


3. (a) The circuit in Figure 3.1 is designed such that the 50 Hz current source delivers maximum power to the load modeled by the resistor R . Find the value of the resistor R for maximum power to be delivered to the load. Hence, find the maximum power absorbed by the load.

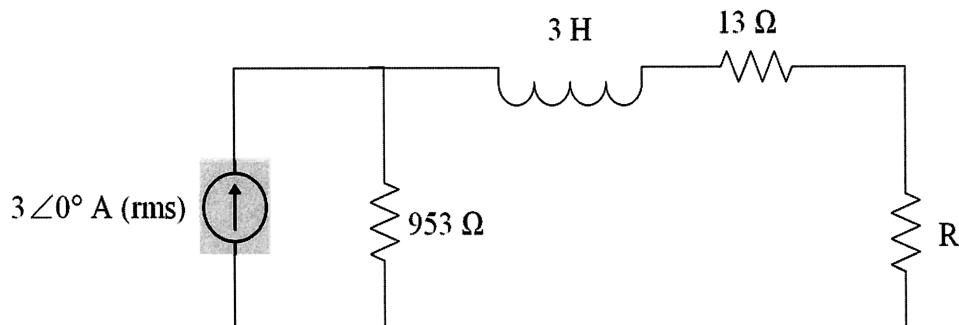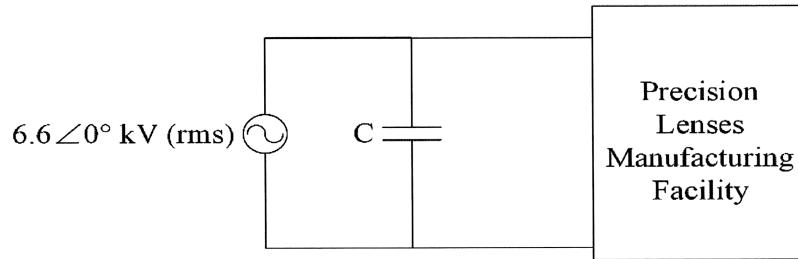**Figure 3.1**

(12 Marks)

Note: Question No. 3 continues on page 4.

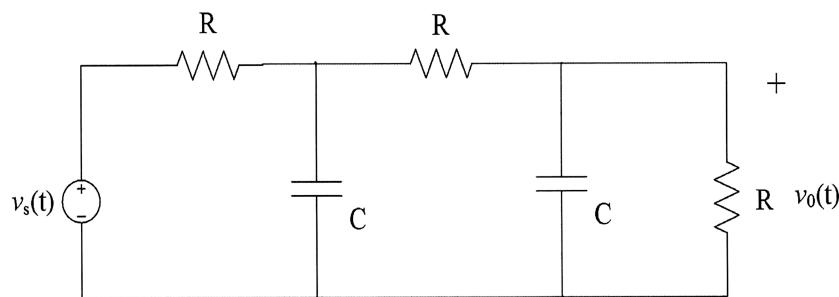
- (b) Electrical power is delivered to a Precision Lenses Manufacturing Facility as shown in Figure 3.2. The frequency of voltage source is 50 Hz. The Precision Lenses Manufacturing Facility has the following loads:
- Highly inductive loads absorbing 13700 kVAR at a power factor of 0.59.
 - Inductive loads absorbing 9800 kW at a power factor of 0.73 lagging.
 - Capacitive loads absorbing 930 kVA at a power factor of 0.55 leading.

**Figure 3.2**

- Find the total complex power of the Precision Lenses Manufacturing Facility.
- Find the reactive power supplied by the capacitor C in Figure 3.2 that will correct the power factor to 0.95 lagging as seen by the 6.6 kV voltage source.

(13 Marks)

4. (a) Find the transfer function $V_o(s)/V_s(s)$ for the circuit shown in Figure 4.1.


**Figure 4.1**

Suppose $v_s(t) = 9u(t)$. Hence find the value of $v_o(t = \infty)$.

(12 Marks)

Note: Question No. 4 continues on page 5.

- (b) Figure 4.2 shows a balanced 50 Hz wye-connected source with rms voltages supplying power to a balanced delta-connected load. The phase load is $Z_L = (879 + j717) \Omega$ and the transmission line impedance is $Z_T = (9 + j7) \Omega$. Find the line currents and the total complex power supplied by the wye-connected source.

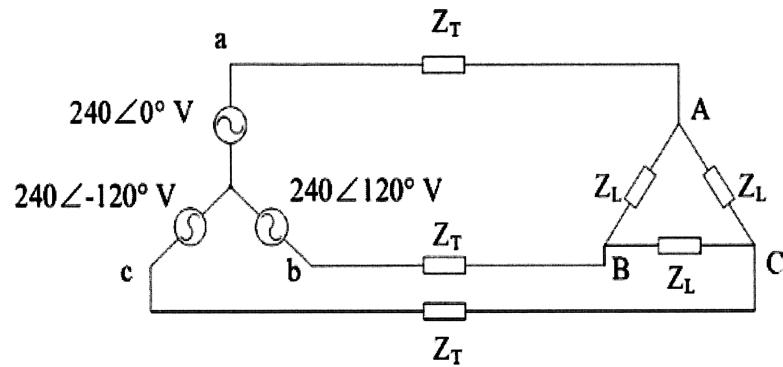**Figure 4.2**

(13 Marks)

Appendix A**Laplace Transform Table**

	$f(t)$	$F(s)$
1. Unit impulse	$\delta(t)$	1
2. Unit step	$u(t)$	$\frac{1}{s}$
3. Unit ramp	$r(t) = tu(t)$	$\frac{1}{s^2}$
4. Unit parabola	$p(t) = \frac{1}{2}t^2u(t)$	$\frac{1}{s^3}$
5. Exponential	e^{-at}	$\frac{1}{s+a}$
6. t-Multiplication exponential	te^{-at}	$\frac{1}{(s+a)^2}$
7. Sine	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
8. Cosine	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
9. Damped Sine	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
10. Damped Cosine	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
11. Linearity	$c_1f_1(t) + c_2f_2(t)$	$c_1F_1(s) + c_2F_2(s)$
12. Differentiation	$\frac{d}{dt}f(t)$	$sF(s) - f(0)$
13. n-Fold differentiation	$\frac{d^n}{dt^n}f(t)$	$s^n F(s) - s^{n-1}f(0) - s^{n-2}f'(0) - \dots - sf^{(n-2)}(0) - f^{(n-1)}(0)$
14. Integration	$\int_{0^-}^t f(\tau)d\tau$	$\frac{F(s)}{s}$
15. t-Multiplication	$tf(t)$	$-\frac{d}{ds}F(s)$

Note: Laplace Transform Table continues on page 7.

Appendix A (continued)
Laplace Transform Table (continued)

	$f(t)$	$F(s)$
16. n-Fold t-Multiplication	$t^n f(t)$	$(-1)^n \frac{d^n}{ds^n} F(s)$
17. Time shift	$f(t - t_0)u(t - t_0);$ $t_0 > 0$	$e^{-s_0 t} F(s)$
18. Frequency shift	$e^{-s_0 t} f(t)$	$F(s + s_0)$
19. Time-frequency scaling	$f(ct) ; c > 0$	$\frac{1}{c} F\left(\frac{s}{c}\right)$
20. Periodic Function	$\begin{aligned} f(t) = & f_1(t)u(t) \\ & + f_1(t-T)u(t-T) \\ & + f_1(t-2T)u(t-2T) + \dots \end{aligned}$	$\frac{1}{1 - e^{-sT}} F_1(s)$

END OF PAPER

EE2101 CIRCUIT ANALYSIS

Please read the following instructions carefully:

- 1. Please do not turn over the question paper until you are told to do so. Disciplinary action may be taken against you if you do so.**

2. You are not allowed to leave the examination hall unless accompanied by an invigilator. You may raise your hand if you need to communicate with the invigilator.

3. Please write your Matriculation Number on the front of the answer book.

4. Please indicate clearly in the answer book (at the appropriate place) if you are continuing the answer to a question elsewhere in the book.